

CISC260 Machine Organization and Assembly Language

Boolean logic, Gates, NAND
universality

Any function can be implemented in Boolean logic.

- Function is a mapping from input variables \mathbf{I} to output value \mathbf{O} .

$$\mathbf{F}: \mathbf{I} \rightarrow \mathbf{O},$$

where $\mathbf{I} \in \{0,1\}^N$, $\mathbf{O} \in \{0,1\}^M$.

Handwritten notes:

A 1
B 1
C 1

+)

X Y
carry sum

Inputs	Output
<u>ABC</u>	<u>XY</u>
<u>000</u>	<u>00</u>
<u>001</u>	<u>01</u>
<u>010</u>	01
<u>011</u>	<u>10</u>
<u>100</u>	01
101	10
110	10
<u>111</u>	<u>11</u>

- Boolean logic

- Boolean variables
- Boolean operators

AND (&), OR (|), NOT(~)

$$Y = \text{AND}(A, B) = A \& B$$

$$Y = \text{OR}(A, B) = A | B$$

$$Y = \text{NOT}(A) = \sim A$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

A	Y
0	1
1	0

Boolean expressions: *made of Boolean variables and Boolean operators much like arithmetic expressions.*

Boolean variables: take values $\{0, 1\}$ or $\{F, T\}$.

Boolean operators:

- $(\& : .)$
- $(| : + \text{ module } 2)$
- $(\sim : . (-1))$

E.g., $Y = A \& B | C \& \sim B$

Precedence(high to low): \sim , $\&$, $|$

Meaning of a Boolean Expression

- Each such expression implies a truth table
→ performs a particular function

- E.g.* $Y = A \& B \mid C \& \sim B$



A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Canonical representation

every Boolean function (defined in a truth can be expressed using at least one Boolean expression called the canonical representation.

Start with a truth table

Procedure:

- And together all literals (negate if 0) in each row (conjunct)
- Or together rows that have true output
- Repeat for each output bit of the function.

The Boolean expression thus obtained is called the “sum-of-product” canonical form.

权威的，牧师的，依教规的

Conclusion: Every Boolean function, no matter how complex, can be expressed using three Boolean operators: AND, OR and NOT.

Boolean Logic Example

Conjuncts:

$\sim A \& \sim B \& \sim C$

$\sim A \& \sim B \& C$

$\sim A \& B \& \sim C$

$\sim A \& B \& C$

$A \& \sim B \& \sim C$

$A \& \sim B \& C$

$A \& B \& \sim C$

$A \& B \& C$

Inputs ABC	Output XY
000	01
001	00
010	00
<u>011</u>	<u>10</u>
<u>100</u>	<u>10</u>
101	00
<u>110</u>	<u>11</u>
111	00

define x first: x
could be — 1.

$\sim A \& B \& C$ |
 $A \& \sim B \& \sim C$ |
 $A \& B \& \sim C$

define y: y could
be — $\sim A \& \sim B \& \sim C$

|
 $A \& B \& \sim C$

Boolean Logic Example

Conjuncts:

$\sim A \& \sim B \& \sim C$

$\sim A \& \sim B \& C$

$\sim A \& B \& \sim C$

$\sim A \& B \& C$

$A \& \sim B \& \sim C$

$A \& \sim B \& C$

$A \& B \& \sim C$

$A \& B \& C$

Inputs	Output
ABC	XY
000	01
001	00
010	00
011	10
100	10
101	00
110	11
111	00

$X = \sim A \& B \& C$

| $A \& \sim B \& \sim C$

| $A \& B \& \sim C$

Boolean Logic Example

- Conjuncts:

$\sim A \& \sim B \& \sim C$

$\sim A \& \sim B \& C$

$\sim A \& B \& \sim C$

$\sim A \& B \& C$

$A \& \sim B \& \sim C$

$A \& \sim B \& C$

$A \& B \& \sim C$

$A \& B \& C$

Inputs	Output	
ABC	XY	
000	01	$X = \sim A \& B \& C$ $A \& \sim B \& \sim C$ $A \& B \& \sim C$
001	00	
010	00	
011	10	$Y = \sim A \& \sim B \& \sim C$ $A \& B \& \sim C$
100	10	
101	00	
110	11	
111	00	

Boolean Logic Example

Inputs	Output
ABC	XY
000	01
001	00
010	00
011	10
100	10
101	00
110	11
111	00

$X = \sim A \& B \& C \mid A \& \sim B \& \sim C \mid A \& B \& \sim C$

$Y = \sim A \& \sim B \& \sim C \mid A \& B \& \sim C$

Alternative Procedure:

OR together all literals (negate if true) in each row
AND together rows that have false output
Repeat for each output bit of the function.

The semantic/syntax needs to be
consistent

The Boolean expression thus obtained has the so-called the “product-of-sum” form.

This procedure works for the same reason that the canonical procedure works.

Just look at the truth tables for AND, OR. They are “identical” in the sense that AND to 1 is just like OR to 0, vice versa.
Namely, AND has value 1 iff all input values are 1, and OR has value 0 iff all input values are 0.

Therefore, this alternative procedure is to define the output from the zero’s perspective.

NB: equivalence of sum-of-product and product-of-sum can also be proved using DeMorgan’s Law. (though the logic could be the other way around, or circular.)

The number of Boolean functions that can be defined over n Boolean variables is 2^{2^n}

2 variables, each variable could have 2 values-0 and 1




All Boolean functions of 2 variables

the function you can define grows exponentially

Function	x	0	0	1	1
	y	0	1	0	1
Constant 0	0	0	0	0	0
And	$x \cdot y$	0	0	0	1
x And Not y	$x \cdot \bar{y}$	0	0	1	0
x	x	0	0	1	1
Not x And y	$\bar{x} \cdot y$	0	1	0	0
y	y	0	1	0	1
Xor	$x \cdot \bar{y} + \bar{x} \cdot y$	0	1	1	0
Or	$x + y$	0	1	1	1
Nor	$\overline{x + y}$	1	0	0	0
Equivalence	$x \cdot y + \bar{x} \cdot \bar{y}$	1	0	0	1
Not y	\bar{y}	1	0	1	0
If y then x	$x + \bar{y}$	1	0	1	1
Not x	\bar{x}	1	1	0	0
If x then y	$\bar{x} + y$	1	1	0	1
Nand	$\overline{x \cdot y}$	1	1	1	0
Constant 1	1	1	1	1	1

Gates implement Boolean logic

   - Physical, Boolean Operator
 - A physical entity that implements a small truth table
 - *E.g.* AND, OR, NOT








How to wire the gates according to a Boolean expression?

- Can implement any Boolean expression with a collection of gates
 1. Find outer-most operator Lowest precedence logical operator
 2. Replace with gate
 3. Work recursively on input functions



Example

- $Y = A \& B \mid C \& \sim B$

     


Any Function in Gates

- Combining: we can
 - Express any function with Boolean expressions
 - Implement any Boolean expression with gates
- Can implement any function with gates

NAND gate universality

 
- NAND gate AND gate followed by a negation



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

- Universality: Any Boolean expression can be implemented using NAND gates only.


- NOT gate

 

- AND gate




- OR gate

 

A	B	$\sim(A \& B)$	$A B$	$\sim A$	$\sim B$	$\sim(\sim A \& \sim B)$
0	0	1	0	1	1	0
0	1	1	1	1	0	1
1	0	1	1	0	1	1
1	1	0	1	0	0	1

From the truth table, we see $A|B = \sim(\sim A \& \sim B)$,
which means

 


If we let $\sim A = C$ and $\sim B = D$, then we have $\sim(C \& D) = (\sim C)|(\sim D)$, which is DeMorgan's Law.


DeMorgan's Law: $\sim(A \& B) = \sim A \mid \sim B$

“Not A and B means neither A nor B”

 Start with the left hand side, it is a NAND gate with inputs A, B.



 Negate the input twice is still equal to the input itself. That is, $\sim\sim A = A$. Recognize the OR gate implemented by 3 NAND gates.



To simplify logic/circuit design

- Identity law: $A + 0 = A$ and $A \cdot 1 = A$.
- Zero and One laws: $A + 1 = 1$ and $A \cdot 0 = 0$.
- Inverse laws: $A + \bar{A} = 1$ and $A \cdot \bar{A} = 0$.
- Commutative laws: $A + B = B + A$ and $A \cdot B = B \cdot A$.
- Associative laws: $A + (B + C) = (A + B) + C$ and $A \cdot (B \cdot C) = (A \cdot B) \cdot C$.
- Distributive laws: $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ and $A + (B \cdot C) = (A + B) \cdot (A + C)$.

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$\overline{(x + y)} = \bar{x} \cdot \bar{y}$$

DeMorgan's Law

Simplifying logic

e.g.,

$$Y = A \& B \mid A \mid C$$



$$= AB + A + C$$

$$= A(B+1) + C \quad \text{distribution, identity}$$

$$= A(1) + C \quad \text{law of 1's}$$

$$= A + C \quad \text{identity}$$

$$= A \mid C$$

  

K-map

- Logic optimization
 - Very difficulty: NP-complete
 - Commercial software

Summary

- Any function on binary input/output can be implemented in Boolean logic
- Boolean logic can be implemented by physical devices – gates.
- Logic gates, as an abstraction, hide the physical details of the devices.
- Only need a small number of primitive gates, actually, only a single gate type NAND2 is enough.