

Build A Simple Computer

1. Any function defined on binary input and output variables can be implemented as Boolean expression. True or False?

- A. True
- B. False


2. Which of the following is the canonical expression for XOR?

A. $Y = \sim (A \mid B)$


B. $Y = \sim A \mid \sim B$

C. $Y = \sim A \& B$

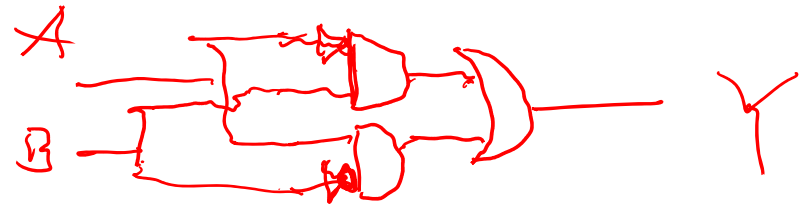D. $Y = (\sim A \& B) \mid (A \& \sim B)$



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

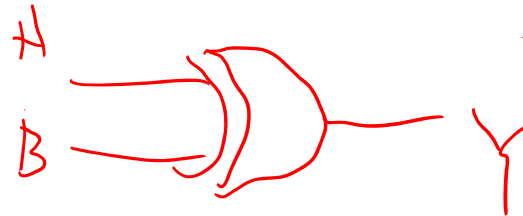


1 Half Adder

$C = \text{Carry}$
 $S = \text{sum}$

$$\begin{array}{r} a \\ + b \\ \hline C \ S \end{array}$$



a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = f(a, b) = \text{XOR}(a, b)$$

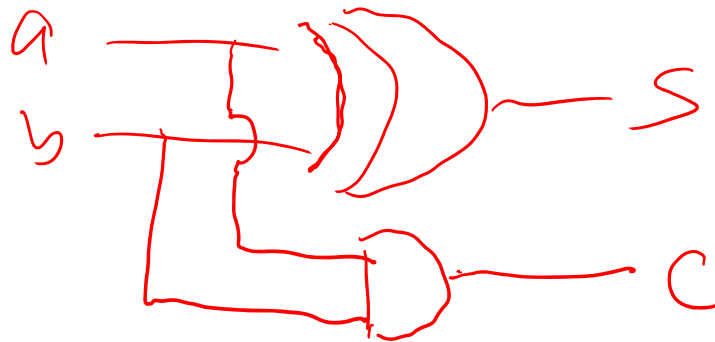

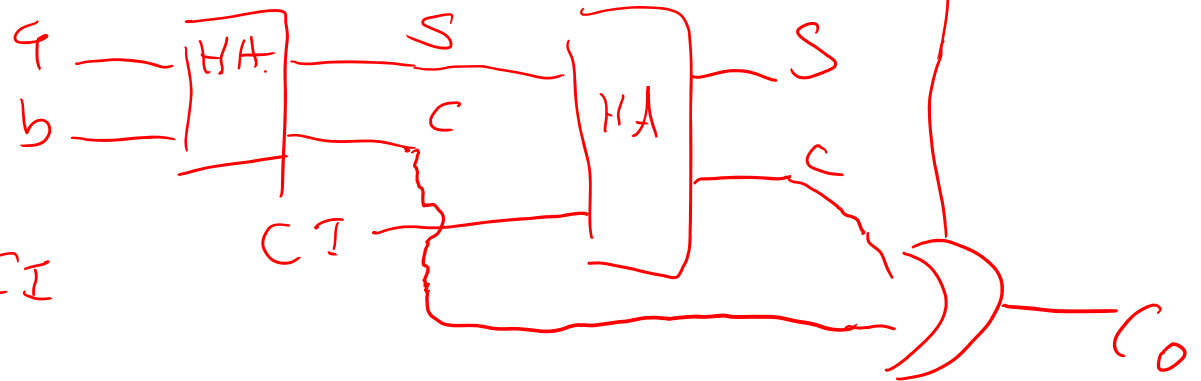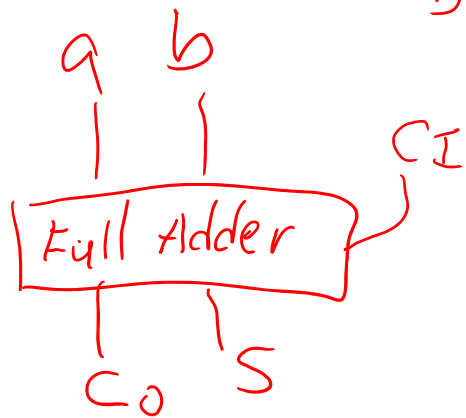2. Full Adder


$$\begin{array}{r}
 \\
 \\
 \hline
 Co
 \end{array}$$




a	b	CI	S	Co
1	1	1	1	1

3, Adder

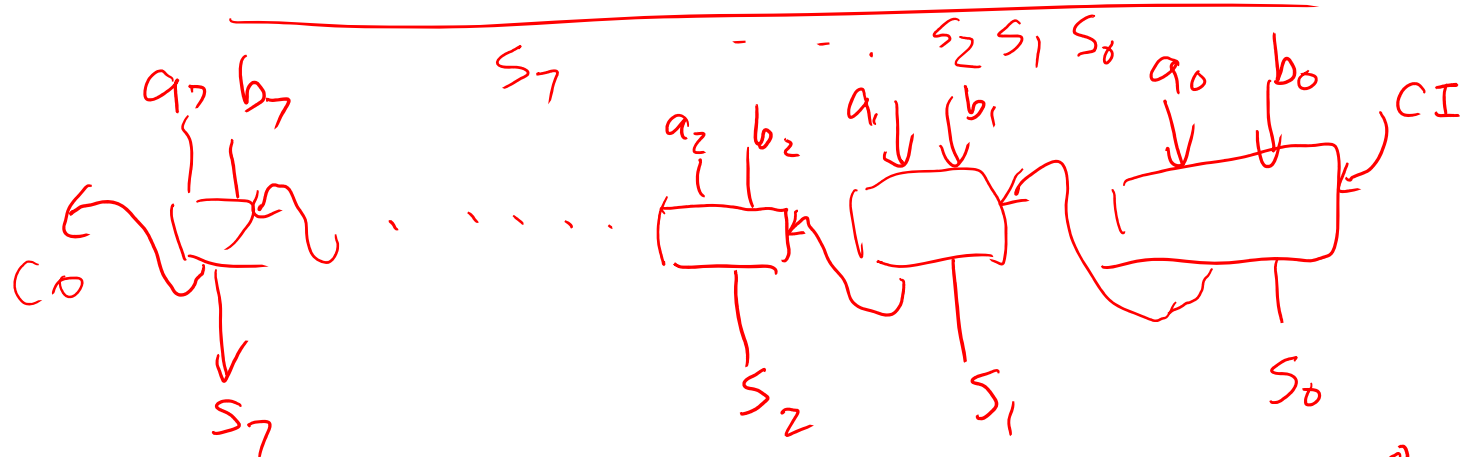
$$\begin{array}{r}
 a_7 a_6 a_5 a_4 a_3 a_2 a_1 a_0 \\
 +) \quad b_7 b_6 \dots \dots \dots - b_0 \\
 \hline
 \end{array}$$



Ripple Adder

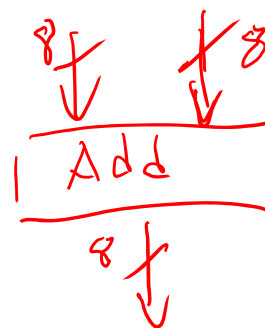

4. Decoder

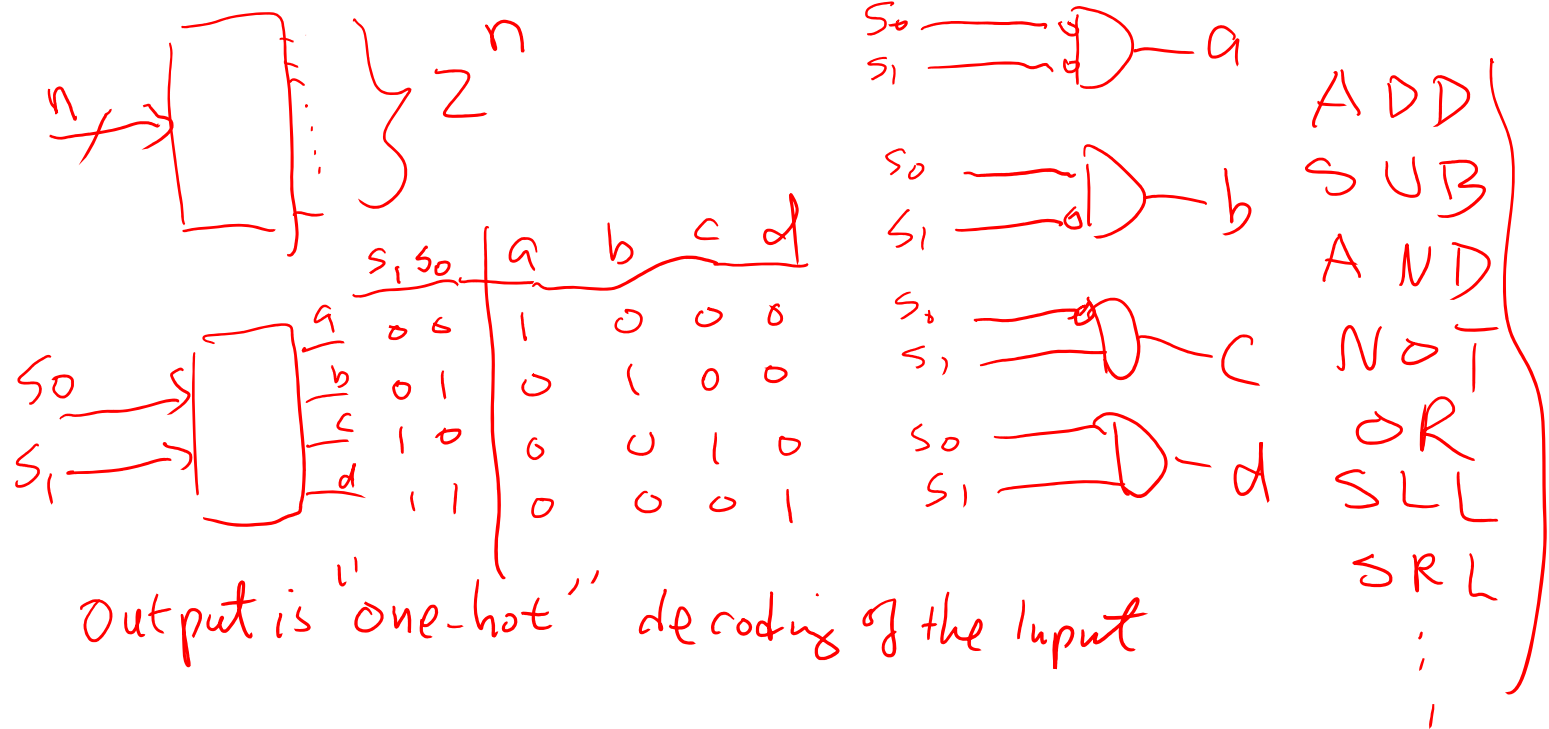

3. Which of the following is the canonical expression for the function defined by the following truth table?

A. $Y = A \cdot \sim B \cdot \sim S$

B. $Y = A \cdot B \cdot \sim S$

C. $Y = \sim A \cdot B \cdot S$

D. $Y = A \cdot B \cdot S$

E. $Y = A \cdot \sim B \cdot \sim S + A \cdot B \cdot \sim S + \sim A \cdot B \cdot S + A \cdot B \cdot S$


multiplexer

X: don't care

A	B	S	Y
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

\Rightarrow

A	B	S	Y
A	X	0	A
X	B	1	B

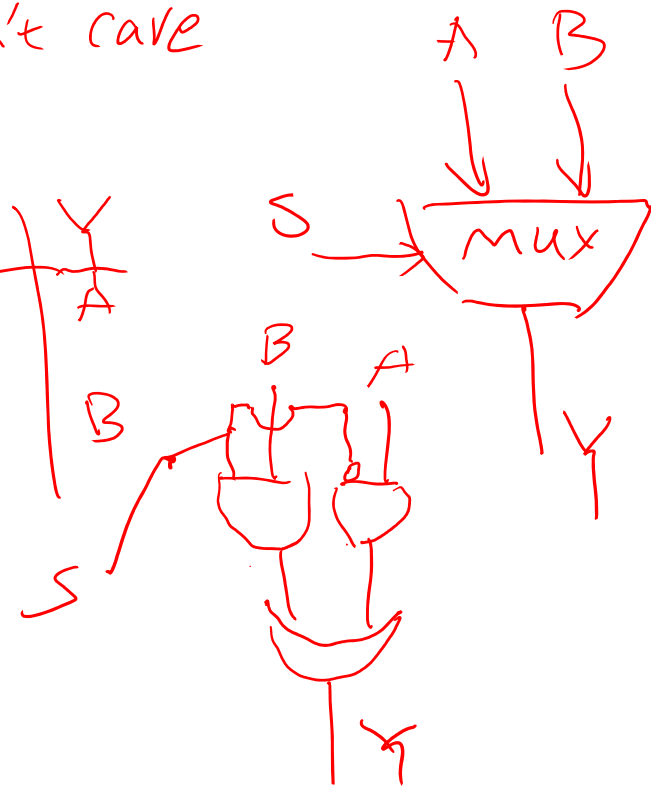

4. Are the following two Boolean expressions equivalent to each other for the function $Y = f(A,B,S)$ defined by the following truth table?


$$Y = A \& \sim S \mid B \& S$$

$$Y = A \& \sim B \& \sim S \mid A \& B \& \sim S \mid \sim A \& B \& S \mid A \& B \& S$$

A	B	S	Y
<hr/>			
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

A. Yes

B. No

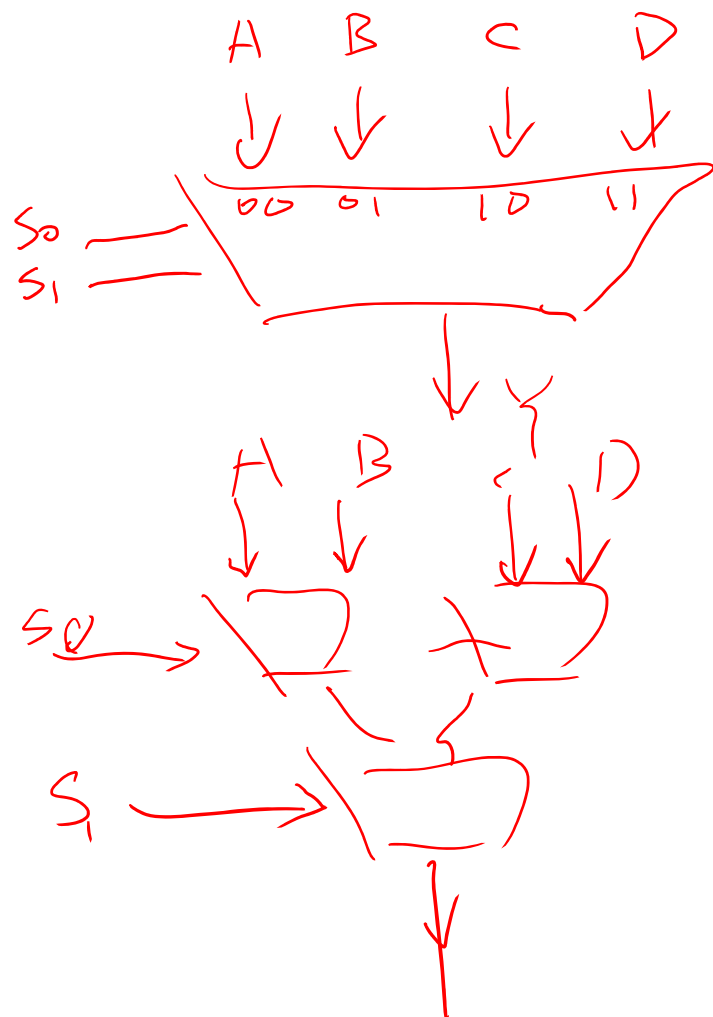


A	B	C	D	S ₀	S ₁	Y
A	x	x	x	0	0	A
x	B	x	x	0	1	B
x	x	C	x	1	0	C
x	x	x	D	1	1	D



opcode

	opcode
ADD	0000
SUB	0001
...	...

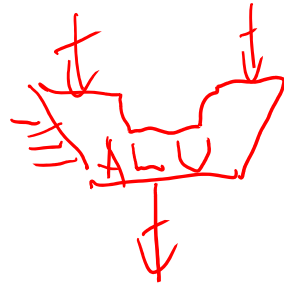

Programmable!!